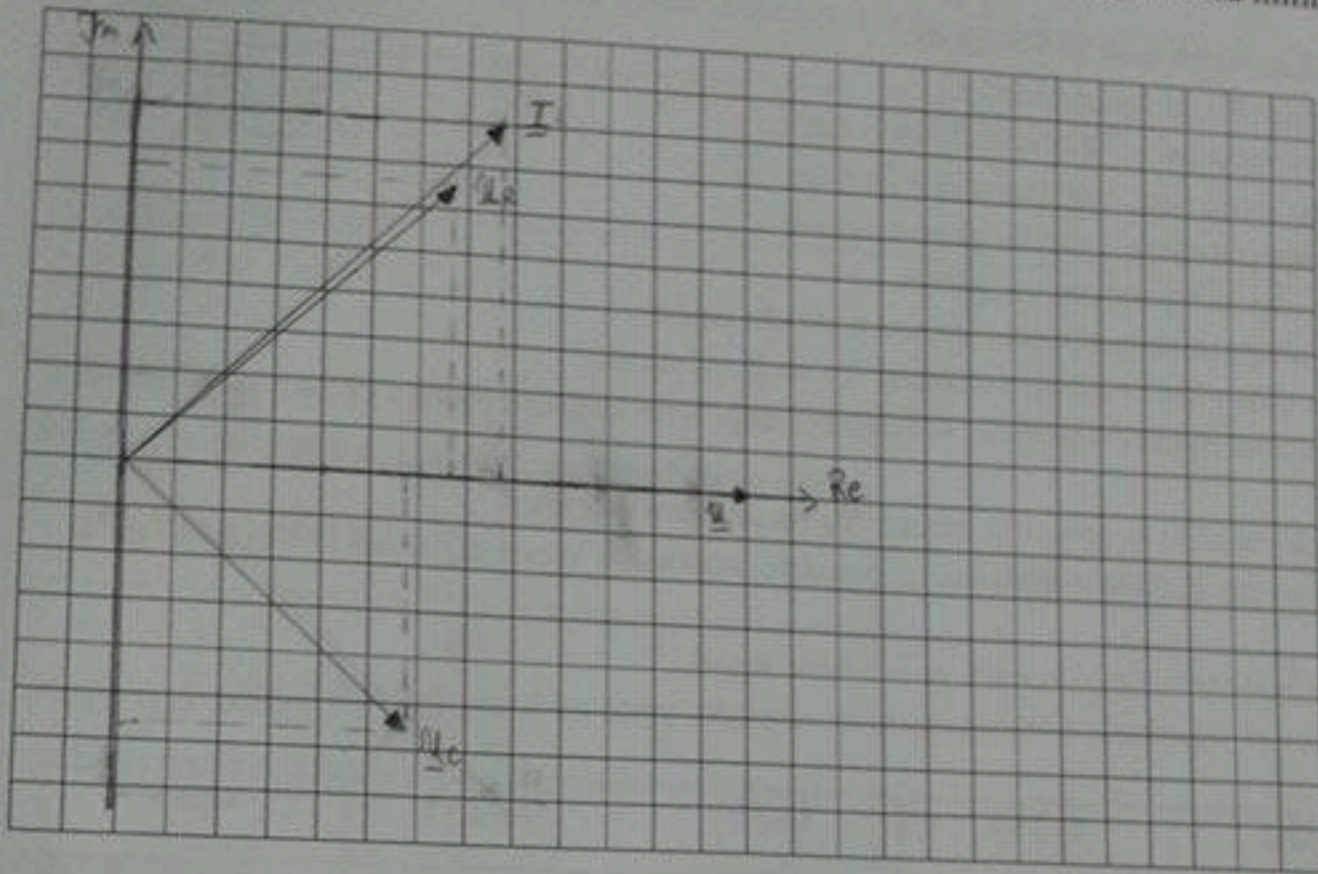


Prema za vježbu 1: Prije dolaska na vježbu potrebno je da studenti proračunski odrede sljedeće veličine naizmjeničnog kruga, uzimajući u obzir da je  $\underline{U} = 30e^{j0}$ :

Tražena veličina	Relacija	Fazor veličine	Efektivna vrijednost
Ukupna impedansa el. kruga	$Z = Z_R + Z_C = R - jX_C = R - \frac{1}{j\omega C}$	$Z = 200 - j199,04 [\Omega] = 282,165 \cdot e^{-j44,86^\circ} [\Omega]$	$Z = \sqrt{200^2 + 199,04^2} = 282,16 [\Omega]$
Struja u el. krugu	$I = \underline{U} / Z_{ek}$	$I = 30 \cdot e^{j0} / 282,165 \cdot e^{-j44,86^\circ} = 0,106 \cdot e^{j44,86^\circ} [A]$	$I = \sqrt{0,075^2 + 0,07476^2} = 0,106 [A]$
Napona na kondenzatoru	$\underline{U}_C = I \cdot Z_C$	$\underline{U}_C = 0,106 \cdot e^{j44,86^\circ} \cdot 199,04 \cdot e^{-j90^\circ} = 21,09 \cdot e^{-j45,14^\circ} [V]$	$U_C = 21,09 [V]$
Napona na aktivnom otporu	$\underline{U}_R = I \cdot Z_R$	$\underline{U}_R = 0,106 \cdot e^{j44,86^\circ} \cdot 200 \cdot e^{j0^\circ} = 21,26 \cdot e^{j44,86^\circ} [V]$	$U_R = 21,26 [V]$
Napona na otporaču	$\underline{U}_{RC} = \underline{U}_R + \underline{U}_C$	$\underline{U}_{RC} = 21,26 \cdot e^{j44,86^\circ} + 21,09 \cdot e^{-j45,14^\circ} = 15,017 + j14,99 + 14,88 - j14,94 = 29,92 + j0,05 [V] = 29,92 \cdot e^{j0,095^\circ} [V]$	$U_{RC} = 29,92 [V]$

Tražena veličina	Relacija	Vrijednost
Kosinus snage el. kruga	$\cos\varphi = P /  S  = P / \sqrt{P^2 + Q^2}$ $S = \underline{U}_{RC} \underline{I}^*$ $P = \text{Re}\{\underline{U}_{RC} \underline{I}^*\}$	0,7088
Kutni faznog pomaka između napona izvora i struje u el. krugu	$\varphi = \varphi_I - \varphi_U$	44,86°


Nacrtati fazorski dijagram za računске veličine na priloženom dijagramu sa milimetarskom (5 x 5 mm) podjelom.



$$1 \text{ mm} = 0,5 \text{ V}$$

$$1 \text{ mm} = 2 \text{ mA}$$

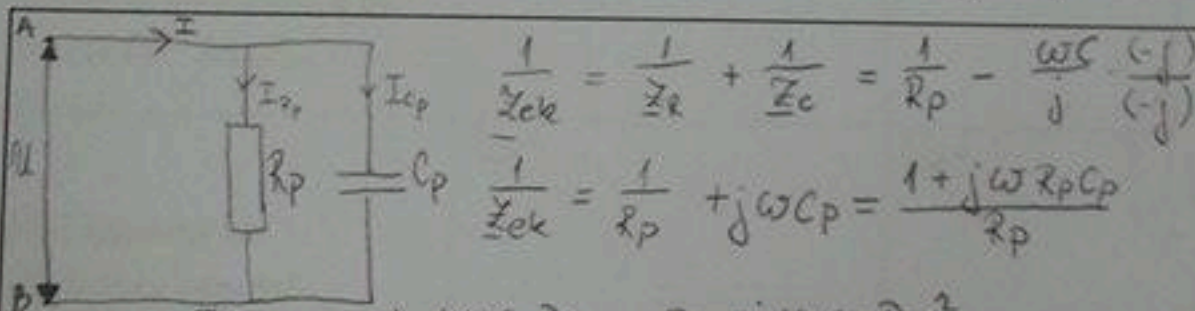Odrediti proračunski vrijednost otpora  $R_p$  i kapacitet kondenzatora  $C_p$ , koji bi paralelno spojeni davali istu ukupnu struju u krugu pri istom naponu izvora (ukupna impedansa u kolu treba biti ista):



$$\frac{1}{Z_{ek}} = \frac{1}{Z_R} + \frac{1}{Z_C} = \frac{1}{R_p} - \frac{j\omega C_p}{(-j)}$$

$$\frac{1}{Z_{ek}} = \frac{1}{R_p} + j\omega C_p = \frac{1 + j\omega R_p C_p}{R_p}$$

$$Z_{ek} = \frac{R_p}{1 + j\omega C_p R_p} \cdot \frac{1 - j\omega C_p R_p}{1 - j\omega C_p R_p} = \frac{R_p - j\omega C_p R_p^2}{1 + \omega^2 R_p^2 C_p^2}$$

$$\begin{matrix} 200 & -j199,04 \\ (\text{Re}) & (\text{Im}) \end{matrix} = \begin{matrix} R_p \\ 1 + \omega^2 R_p^2 C_p^2 \end{matrix} - j \frac{\omega C_p R_p^2}{1 + \omega^2 R_p^2 C_p^2}$$

$$200 = \frac{R_p}{1 + \omega^2 R_p^2 C_p^2} \quad \wedge \quad 199,04 = \frac{\omega C_p R_p^2}{1 + \omega^2 R_p^2 C_p^2}$$

$$\text{Re}\{Z\} \approx \text{Im}\{Z\}$$

$$\frac{R_p}{1 + \omega^2 R_p^2 C_p^2} = 200 \Rightarrow R_p = 400 [\Omega]$$

$$C_p = \frac{1}{\omega R_p} = \frac{1}{314 \cdot 400} \Rightarrow C_p = 7,96 [\mu\text{F}]$$